

EXP NO: 1

Estimation of Characteristic Impedance (Z_0), and Propagation Constant (γ) of a Transmission Line from Primary Constants.

Test Case 1:

Investigating the significance of Characteristic Impedance (Z_0), and Propagation Constant

(γ) of a Transmission Line using the following parameters

Code:

```
clear; clc;
R=10;L=0.003;f=2*10^3;G=4*(10^-6);C=16*(10^-6);
w=2*%pi*f;
Z=R+(%i*w*L);
Y=G+(%i*w*C);
Zo=sqrt(Z/Y);
C=round(real(Zo));
D=round(imag(Zo));
printf('-Zo = %f + j(%f)ohms\n',C,D);
P=sqrt(Z*Y);
a=real(P);
a1=round(a*10000)/10000;
printf('-Attenuation constant a = %f neper/km\n',a1);
b=imag(P);
b1=round(b*10000)/10000;
printf('-Phase constant b = %f radians/km',b1);
```

OUTPUT:

Simulation results			Theoretical results	
Z0(ohms)	α (neper/km)	β (radians/km)	α (neper/km)	β (radians/km)
	0.33	2.99	0.2378	4.421

THEORETICAL RESULTS:

Given,

$$R = 10\Omega$$

$$C = 8\mu F$$

$$L = 3.5mH$$

$$G = 4\mu mho$$

$$F = 2kHz$$

$$\omega = 2\pi f$$

$$= 2\pi \times 2 \times 10^3$$

$$\omega = 12566.37$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{10+j(12566.37)(0.0035)}{4 \times 10^{-6} + j(12566.37)(8 \times 10^{-6})}}$$

$$Z_0 = \sqrt{\frac{10+j43.98}{0.000004+j0.10053}}$$

$$Z_0 = 20.95 - j2.17\Omega$$

$$|Z_0| = \sqrt{(20.95)^2 + (2.17)^2}$$

$$Z_0 = 21.06\Omega$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\gamma = \sqrt{(10+j43.98)(0.000004+j0.10053)}$$

$$\gamma = 0.2378 + j4.421$$

$$\alpha = 0.2378 \text{ nepers/km}, \beta = 4.421 \text{ rad/km}$$

SIMULATION RESULTS:

Scilab code:	Result:
<pre> 1 clear; clc; 2 R=10;L=0.0035;f=2*10^3;G=4*(10^-6);C=16*(10^-6); 3 w=2*pi*f; 4 Z=R+(%i*w*L); 5 Y=G+(%i*w*C); 6 Zo=sqrt(Z/Y); 7 C=round(real(Zo)); 8 D=round(imag(Zo)); 9 printf('-Zo = %f + j(%f)ohms\n',C,D); 10 P=sqrt(Z*Y); 11 a=real(P); 12 a1=round(a*10000)/10000; 13 printf('-Attenuation constant a = %f neper/km\n',a1); 14 b=imag(P); 15 b1=round(b*10000)/10000; 16 printf('-Phase constant b = %f radians/km',b1); </pre>	<pre> -Zo = 15.000000 + j(-2.000000)ohms -Attenuation constant a = 0.336000 neper/km -Phase constant b = 2.992700 radians/km </pre>

TEST CASE 2:

Examine the impact of resistance and inductance on the significance of Characteristic Impedance (Z_0) and Propagation Constant (γ) of a Transmission Line at a frequency $f=2.5$ Khz. Vary the resistance value from $10\ \Omega$ to $50\ \Omega$ at the interval of $10\ \Omega$ with L,G and C values constant and calculate the Characteristic Impedance and Propagation Constant .Vary the inductance values from 3.5 mH to 11.5 mH at the interval of 2.5 mH with R,G and C values constant.

PROGRAM:

```
clear; clc;
R=10;L=0.003;f=2*10^3;G=4*(10^-6);C=16*(10^-6);
w=2*pi*f;
Z=R+(i*w*L);
Y=G+(i*w*C);
Zo=sqrt(Z/Y);
C=round(real(Zo));
D=round(imag(Zo));
printf('-Zo = %f + j(%f)ohms\n',C,D);
P=sqrt(Z*Y);
a=real(P);
a1=round(a*10000)/10000;
printf('-Attenuation constant a = %f neper/km\n',a1);
b=imag(P);
b1=round(b*10000)/10000;
```

OUTPUT:

Variable R

Constants L=3mH; f=2000; G=.4*(10^-6); C=8*(10^-6).

S.No	(R) (Ω)	Theoretical (Z_0) (Ω)	Theoretical α	Theoretical β	Simulation α	Simulation β
1	10	$19.53 - j2.546$	0.2560	1.9635	0.2560	1.9635
2	20	$19.994 - j4.975$	0.5002	2.0100	0.5002	2.0100
3	30	$20.667 - j7.220$	0.7258	2.0777	0.7258	2.0777
4	40	$21.468 - j9.267$	0.9316	2.1582	0.9316	2.1582
5	50	$22.337 - j11.133$	1.1192	2.2456	1.1192	2.2456

Variable L

Constants $R=10\Omega$; $f=2000$; $G=.4*(10^{-6})$; $C=8*(10^{-6})$.

S.No	(L) (mH)	Theoretical (Z_0) (Ω)	Theoretical α	Theoretical β	Simulation α	Simulation β
1	3.5	$21.050 - j2.363$	0.2375	2.1161	0.2375	2.1161
2	8	$31.662 - j1.571$	0.1579	3.1830	0.1579	3.1830
3	6	$27.446 - j1.812$	0.1822	2.7592	0.1822	2.7592
4	11	$37.105 - j1.340$	0.1348	3.7302	0.1348	3.7302
5	11.5	$37.937 - j1.311$	0.1318	3.8138	0.1318	3.8138

SIMULATION RESULT:

Scilab code:

```

1 clear; clc;
2 R=20;L=0.003;f=2*10^3;G=4*(10^-6);C=16*(10^-6);
3 w=2*pi*f;
4 Z=R+(%i*w*L);
5 Y=G+(%i*w*C);
6 Zo=sqrt(Z/Y);
7 C=round(real(Zo));
8 D=round(imag(Zo));
9 printf('-Zo = %f + j(%f)ohms\n',C,D);
10 P=sqrt(Z*Y);
11 a=real(P);
12 a1=round(a*10000)/10000;
13 printf('-Attenuation constant a = %f neper/km\n',a1);
14 b=imag(P);
15 b1=round(b*10000)/10000;
16
17 printf('-Phase constant b = %f radians/km',b1);

```

Result:

```

-Zo = 14.000000 + j(-4.000000)ohms
-Attenuation constant a = 0.707400 neper/km
-Phase constant b = 2.842600 radians/km

```

THEORETICAL RESULT:

Given, $L = 3\text{mH}$
 $f = 2000\text{Hz}$
 $G = 0.4 \times 10^{-6}\text{S}$
 $C = 8 \times 10^{-6}\text{F}$
 $R = 10, 20, 30, 40, 50\Omega$

$\omega = 2\pi f = 2 \times 3.14 \times 2000 = 12566.37 \text{ rad/s}$

(i) $Z_0 = \frac{10 + j(12566.37 \times 0.003)}{4 \times 10^{-6} + j(12566.37 \times 8 \times 10^{-6})} = \frac{10 + j37.69}{0.4 \times 10^{-6} + j0.10053}$
 $Z_0 = 19.57$
 $\gamma = \sqrt{(10 + j37.69)(0.4 \times 10^{-6} + j0.10053)}$
 $\alpha = 0.265$
 $\beta = 3.78$
 $\gamma = 0.265 + j3.78$

(ii) $R = 20$
 $Z_0 = \frac{20 + j37.69}{0.4 \times 10^{-6} + j0.10053} \Rightarrow Z_0 = 20.34$
 $\gamma = 0.510 + j3.816$
 $\alpha = 0.510$
 $\beta = 3.186$

(iii) $R = 30$
 $Z_0 = \frac{30 + j37.69}{0.4 \times 10^{-6} + j0.10053}$
 $\gamma = 0.742 + j3.865 \Rightarrow \alpha = 0.742$
 $\beta = 3.862$

(iv) $R = 40$
 $Z_0 = \frac{40 + j37.69}{0.4 \times 10^{-6} + j0.10053}$
 $\gamma = 0.959 + j3.930 \Rightarrow \alpha = 0.959$
 $\beta = 3.930$

(v) $R = 50$
 $Z_0 = \frac{50 + j37.69}{0.4 \times 10^{-6} + j0.10053}$
 $\gamma = 1.162 + j4.009$
 $\alpha = 1.162$
 $\beta = 4.009$

Given, $R = 10\Omega$, $f = 2000\text{Hz}$
 $G = 0.4 \times 10^{-6}$ $C = 8 \times 10^{-6}$

i) $L = 3.5\text{mH}$
 $Z_0 = \frac{10 + j43.98}{0.4 \times 10^{-6} + j0.10053} = 21.07\Omega$
 $\gamma = \sqrt{(10 + j43.98)(0.4 \times 10^{-6} + j0.10053)}$
 $\alpha = 0.248$
 $\beta = 4.418$

ii) $L = 8\text{mH}$
 $Z_0 = \frac{10 + j106.81}{0.4 \times 10^{-6} + j0.10053} = 32.86\Omega$
 $\gamma = \sqrt{(10 + j106.81)(0.4 \times 10^{-6} + j0.10053)}$
 $\alpha = 0.240$
 $\beta = 7.151$

iii) $L = 8\text{mH} + 6\text{mH}$
 $Z_0 = \frac{10 + j165.40}{0.4 \times 10^{-6} + j0.10053} = 32.86 \quad 27.60\Omega$
 $\gamma = \sqrt{(10 + j165.40)(0.4 \times 10^{-6} + j0.10053)}$
 $\alpha = 0.243$
 $\beta = 6.010$

iv) $L = 11\text{mH}$
 $Z_0 = \frac{10 + j138.23}{0.4 \times 10^{-6} + j0.10053} = 37.39\Omega$
 $\gamma = \sqrt{(10 + j138.23)(0.4 \times 10^{-6} + j0.10053)}$
 $\alpha = 0.238$
 $\beta = 8.248$

v) $L = 11.5\text{mH}$
 $Z_0 = \frac{10 + j144.51}{0.4 \times 10^{-6} + j0.10053} = 38.23\Omega$
 $\gamma = \sqrt{(10 + j144.51)(0.4 \times 10^{-6} + j0.10053)}$
 $\alpha = 0.238$
 $\beta = 8.293$

Test Case 3:

Explore the impact of frequency and capacitance on the significance of Characteristic Impedance (Z_0) and Propagation Constant (γ) of a Transmission Line. Vary the frequency from 2KHz to 10 KHz at the interval of 2 KHz with L,R ,G and C values constant and calculate the Characteristic Impedance and Propagation Constant . Vary the capacitance values from 8 μ F to 16 μ F at the interval of 2 μ F with R,G and L values constant.

OUTPUT:

Variable f

Constants L=3mH; f=2000; G=.4*(10⁻⁶); C=8*(10⁻⁶).

S.No	Input (f) (KHz)	Theoretical (Z_0) (Ω)	Theoretical α (neper/km)	Theoretical β (rad/km)	Simulation α (neper/km)	Simulation β (rad/km)
1	2	19.532 – j2.546	0.2560	1.9635	0.2560	1.9635
2	4	19.407 – j1.281	0.2576	3.9021	0.2576	3.9021
3	6	19.384 – j0.855	0.2580	5.8460	0.2580	5.8460
4	8	19.376 – j0.642	0.2581	7.7914	0.2581	7.7914
5	10	19.372 – j0.513	0.2581	9.7373	0.2581	9.7373

Variable c

Constants R=10 Ω ; f=2000; G=.4*(10⁻⁶); C=8*(10⁻⁶).

S.NO	INPUT (C) (μ F)	Theoretical (Z_0) (Ω)	Theoretical α	Theoretical β	Simulation α	Simulation β
1	8	19.532 – j2.546	0.2560	1.9635	0.2560	1.9635
2	10	17.470 – j2.278	0.2862	2.1953	0.2862	2.1953
3	12	15.948 – j2.079	0.3135	2.4048	0.3135	2.4048

S.NO	INPUT (C) (μF)	Theoretical (Z_0) (Ω)	Theoretical α	Theoretical β	Simulation α	Simulation β
4	14	$14.765 - j1.925$	0.3387	2.5975	0.3387	2.5975
5	16	$13.811 - j1.801$	0.3620	2.7769	0.3620	2.7769

SIMULATION RESULT:

Scilab

code:

```

1 clear; clc;
2 R=10;L=0.003;f=2*10^3;G=4*
  (10^-6);C=16*(10^-6);
3 w=2*pi*f;
4 Z=R+(%i*w*L);
5 Y=G+(%i*w*C);
6 Zo=sqrt(Z/Y);
7 C=round(real(Zo));
8 D=round(imag(Zo));
9 printf('-Zo = %f +
  j(%f)ohms\n',C,D);
10 P=sqrt(Z*Y);
11 a=real(P);
12 a1=round(a*10000)/10000;
13 printf('-Attenuation constant a =
  %f neper/km\n',a1);
14 b=imag(P);
15 b1=round(b*10000)/10000;
16 printf('-Phase constant b = %f
  radians/km',b1);

```

Result:

```

-Zo = 14.000000 + j(-2.000000)ohms
-Attenuation constant a = 0.362100
neper/km
-Phase constant b = 2.776900
radians/km

```

Test case 3

$$f = 2 \text{ KHz}$$

$$Z_0 = \sqrt{\frac{10 + j37.70}{0.4 \times 10^6 + j0.10053}}$$

$$Z_0 = 19.53 - j2.546 \Omega$$

$$\gamma = \sqrt{(10 + j37.70)(0.4 \times 10^6 + j0.10053)} = \alpha = 0.256$$

$$\beta = 1.964$$

$$f = 4 \text{ KHz}$$

$$\omega = 25132.74$$

$$Z_0 = 19.407 - j1.281 \Omega$$

$$\gamma = 0.258 + j3.902$$

$$f = 6 \text{ KHz}$$

$$\omega = 37699.11$$

$$Z_0 = \sqrt{\frac{10 + j113.10}{0.4 \times 10^6 + j0.30159}}$$

$$Z_0 = 19.384 - j0.855 \Omega$$

$$\gamma = 0.258 + j5.846 \text{ rad/km}$$

$$f = 8 \text{ KHz}$$

$$\omega = 50265.48$$

$$Z_0 = 19.376 - j0.642 \Omega$$

$$\gamma = 0.258 + j7.791$$

$$f = 10 \text{ KHz}$$

$$\omega = 62831.85$$

$$Z_0 = 19.372 - j0.513 \Omega$$

$$\gamma = 0.258 + j9.373 \text{ rad/km}$$